

# Transistor and Op-Amp Amplifiers: Configurations, Characteristics, and Analysis

Electrical Engineering · Answer Key · 10 Questions

---

**1. What is a key advantage of the common emitter transistor configuration?**

- A) High voltage and current gain**
- B) Low input impedance
- C) High output impedance
- D) No phase shift

**2. In an RC-coupled amplifier, what causes the drop in gain at low frequencies?**

- A) Parasitic capacitances
- B) Increasing reactance of coupling capacitors**
- C) Transistor saturation
- D) Decreasing input impedance

**3. What parameter is used to measure how well an op-amp rejects common-mode signals?**

- A) Slew Rate
- B) CMRR (Common-Mode Rejection Ratio)**
- C) Input Offset Voltage
- D) Thermal Drift

**4. Which type of feedback increases overall gain and can lead to instability in op-amps?**

- A) Negative feedback
- B) Positive feedback**
- C) Series feedback
- D) Shunt feedback

**5. What is the purpose of DC biasing in a transistor amplifier?**

- A) To reduce power consumption
- B) To set the operating point in the active region**
- C) To increase voltage gain
- D) To minimize distortion

**6. What is the effect of Miller capacitance in high-frequency amplifier circuits?**

- A) Increases bandwidth
- B) Decreases input capacitance
- C) Increases input capacitance**
- D) Reduces distortion

**7. What is the relationship between the collector current ( $I_c$ ), base current ( $I_b$ ), and beta ( $\beta$ ) in a BJT?**

- A)  $I_c = I_b / \beta$
- B)  $I_c = I_b + \beta$
- C)  $I_c = \beta * I_b$**
- D)  $I_b = \beta * I_c$

**8. Which amplifier class has the highest theoretical efficiency?**

- A) Class A
- B) Class B
- C) Class AB
- D) Class C**

**9. What does slew rate indicate in op-amps?**

- A) Input impedance
- B) Output impedance
- C) Maximum rate of change of output voltage**
- D) Power consumption

**10. What is the phase shift between the input and output signals in a common emitter amplifier?**

- A) 0 degrees
- B) 90 degrees
- C) 180 degrees**
- D) 360 degrees